

Measuring Power in Three-Phase Circuits

- ❑ Measuring power to a 4-wire Y load requires three wattmeters (one meter per phase)
- ✓ Loads may be balanced or unbalanced
- ✓ Total power is the sum of individual powers
- ✓ If the load could be guaranteed to be balanced
 - Only one meter would be required
 - Its value is multiplied by 3



Measuring Power in Three-Phase Circuits

- For a three-wire system, only two meters are needed
- Loads may be Y- or Δ -connected
- Loads may be balanced or unbalanced
- Total power is the algebraic sum of meter readings

